
VLSI Design : Quiz-1

Monsoon 2024, IIT Hyderabad (Instructor: Prof. Abhishek Srivastava)

Date : 28th Aug, 2024, Duration : 1 Hour, Max. Marks : 10

Instructions:

- Clearly write your assumptions (if any)
 - Use of own hand-written notes on 1 A4 sheet (both sides) is allowed
 - Calculators are allowed
-

1. Derive the input voltage expression for which the static current drawn by the CMOS inverter is maximum? Given: $K_n = K_p$ (where, $K = \mu C_{ox} \frac{W}{L}$), $V_{Tn} = 0.55$ V, $V_{Tp} = -0.65$ V, $\mu_n C_{ox} = 220 \mu\text{A/V}^2$, $V_{DD} = 1.8$ V and $(\frac{W}{L})_n = 10$. What is the value of this maximum current for the given parameters? [2]
2. Consider a CMOS inverter. You are given that $V_{DD} = 3.0$ V, $V_{Tn} = 0.5$ V, $V_{Tp} = -0.7$ V, $\mu_n = 450 \text{ cm}^2/\text{Vs}$, and $\mu_p = 250 \text{ cm}^2/\text{Vs}$. The n and p channel transistors have the same channel length and gate oxide capacitance per unit area and overall capacitance at inverter output is C_L .
 - (a) Derive the expression for the time (τ_r) taken to charge the output from 0 V to $V_{DD} - |V_{Tp}|$ with the input voltage equal to V_{Tn} for which n channel transistor is considered as off. [3]
 - (b) Derive the expression for the time (τ_f) taken to discharge the output from V_{DD} to V_{Tn} with the input voltage equal to $V_{DD} - |V_{Tp}|$ for which p channel transistor is considered as off. [3]
 - (c) Find the ratio $\frac{W_p}{W_n}$ such that $\tau_r = \tau_f$. [2]

Hints:

- i. Identify the mode of operation for the range of output values and use corresponding current equations
- ii. These substitutions might help in simplification:

$$V_1 = V_{Tn} + |V_{Tp}|; V_2 = V_{DD} - V_{Tn} - |V_{Tp}|$$

$$\frac{1}{ay^2 + by} = \frac{1}{b} \left(\frac{1}{y} - \frac{a}{ay + b} \right)$$

$$\int \frac{dy}{ay + b} = \frac{1}{a} \ln(ay + b)$$

$$\int \left(\frac{1}{y} - \frac{a}{ay + b} \right) dy = \ln \frac{y}{ay + b}$$

Good luck !!