

VLSI Design

Tutorial - Icarus Verilog & GTKWave

Prof. Abhishek Srivastava

CVEST, IIIT Hyderabad



INTERNATIONAL INSTITUTE OF
INFORMATION TECHNOLOGY

H Y D E R A B A D

About Icarus Verilog & GTKWave

- ***Icarus Verilog*** is a Verilog simulation and synthesis tool.
 - It operates as a compiler, compiling source code written in Verilog (IEEE-1364) into some target format.
 - For batch simulation, the compiler can generate an intermediate form called vvp assembly. This intermediate form is executed by the “vvp” command.
 - For synthesis, the compiler generates netlists in the desired format.
- ***GTKWave*** is a fully featured GTK+ based wave viewer for Verilog VCD/EVCD files.

Instructions to Install iverilog & GTKWave

- Instructions for **Ubuntu/Linux (Recommended)** :
 - To install iverilog** : Execute the following bash command :
 - *sudo apt-get install iverilog*
 - To install GTKWave** : Execute the following bash command :
 - *sudo apt-get install gtkwave*

Instructions to run iverilog & GTKWave

■ To run iverilog :

- Open the terminal.
- Go to the directory containing the verilog code and testbench
- Type *iverilog -o <output> <testbench.v> <code.v>*.
- To execute the output file on terminal : Type *vvp <output>*.

■ To run GTKWave :

- Open the terminal.
- Go to the directory containing the *< filename.vcd >*.
- Type *gtkwave <filename.vcd> &*.
- In the left pane of the pop-up window, click on the
- Signals appear in the lower left side of the window
- Drag and drop the signals to be viewed in the waveform window
- Go to *Time > Zoom > Zoom Best Fit* to see the whole waveform

Example verilog codes and testbench - 1

■ 1x2 Decoder verilog code

```
`timescale 1ns / 1ps
module two_decoder(a,en,y1,y2);
input a,en;
output y1,y2;
and A1(y1,~a,en);
and A2(y2,a,en);
endmodule
```

Figure: two_decoder.v

■ 1x2 Decoder verilog testbench

```
`timescale 1ns / 1ps|
module two_decoder_test;

// Inputs
reg a;
reg en;

// Outputs
wire y1;
wire y2;

// Instantiate the Unit Under Test (UUT)
two_decoder uut (
    .a(a),
    .en(en),
    .y1(y1),
    .y2(y2)
);

initial begin
    $dumpfile("two_decoder_test.vcd");
    $dumpvars(0,two_decoder_test);
    // Initialize Inputs
    a = 1'b0;
    en = 1'b0;
    #100 $finish;
end

always #5 a = ~a;
always #10 en = ~en;
always@(a)
    $monitor("time = %t \t y1 = %d \t y2 = %d", $time, y1, y2);

endmodule
```

Figure: two_decoder_test.v

Example verilog codes and testbench - 2

■ 1x4 *Demux* verilog code

```
`timescale 1ns / 1ps
module two_demux(y,S,a,b);
input y,S;
output a,b;
and A1(a,~S,y);
and A2(b,S,y);
endmodule

module demux_four(y,S_0,S_1,a,b,c,d);
input y,S_0,S_1;
output a,b,c,d;
wire p,q;
two_demux B1(y,S_1,p,q);
two_demux B2(p,S_0,a,b);
two_demux B3(q,S_0,c,d);
endmodule
```

Figure: four_demux.v

■ 1x4 *Demux* verilog testbench

```
`timescale 1ns / 1ps
module demux_four_test;

// Inputs
reg y;
reg S_0;
reg S_1;

// Outputs
wire a;
wire b;
wire c;
wire d;

// Instantiate the Unit Under Test (UUT)
demux_four uut (
    .y(y),
    .S_0(S_0),
    .S_1(S_1),
    .a(a),
    .b(b),
    .c(c),
    .d(d)
);

initial begin
    // Initialize Inputs
    $dumpfile("demux_four_test.vcd");
    $dumpvars(0,demux_four_test);
    y = 0;
    S_0 = 0;
    S_1 = 0;
    #100 $finish;
end

// Add stimulus here
always #20 y = ~y;
always #5 S_0 = ~S_0;
always #10 S_1 = ~S_1;
always@(y or S_0 or S_1)
$monitor("time = %t y = %d \t a = %d \t b = %d \t c = %d \t d = %d", $time, y, a, b, c, d);

endmodule
```

Figure: four_demux_test.v

Example verilog codes and testbench - 3

■ *D – Flipflop* verilog code

```
`timescale 1ns / 1ps
module dff(clk,rst,D,Q);
input clk,rst,D;
output reg Q;
always@(posedge clk or negedge rst)
begin
if(!rst)
Q <= 1'b0;
else
Q <= D;
end
endmodule
```

Figure: dff.v

■ *D – Flipflop* verilog testbench

```
`timescale 1ns / 1ps
module dff_test;

// Inputs
reg clk;
reg rst;
reg D;

// Outputs
wire Q;

// Instantiate the Unit Under Test (UUT)
dff uut (
.clk(clk),
.rst(rst),
.D(D),
.Q(Q)
);

initial begin
// Initialize Inputs
$dumpfile("dff_test.vcd");
$dumpvars(0,dff_test);
clk = 1;
rst = 0;
D = 0;
#100 $finish;
end

always #5 clk = ~clk;
always#20 rst = ~rst;
always#10 D = ~D;
always@(D or rst)
$monitor("time = %t \t rst = %b \t D = %b \t Q = %b", $time, rst, D, Q);
endmodule
```

Figure: dff_test.v

Executing 1x2 Decoder

- Using **iverilog**
 - Open the terminal
 - Go to the directory containing verilog codes
 - Type *iverilog -o two_dec two_decoder_test.v two_decoder.v*
 - Type *vvp two_dec*
- Using **GTKWave**
 - In the terminal type *gtkwave two_decoder_test.vcd* &
 - Click on *two_decoder_test* in the left pane of the pop up window
 - Drag and drop all the signals into waveform window
 - Go to *Time > Zoom > Zoom Best Fit* to see the whole waveform

```
karishkaran@karishkaran:~/Documents/Decoder$ iverilog -o two_dec two_decoder_test.v two_decoder.v
karishkaran@karishkaran:~/Documents/Decoder$ vvp two_dec
INFO: dumpfile two_decoder_test.vcd speed for output.
time = 0 p1 = 0 p2 = 0
time = 5000 p1 = 1 p2 = 0
time = 10000 p1 = 0 p2 = 1
time = 15000 p1 = 0 p2 = 1
time = 20000 p1 = 0 p2 = 0
time = 25000 p1 = 0 p2 = 0
time = 30000 p1 = 1 p2 = 0
time = 35000 p1 = 1 p2 = 1
time = 40000 p1 = 0 p2 = 0
time = 45000 p1 = 0 p2 = 0
time = 50000 p1 = 1 p2 = 0
time = 55000 p1 = 0 p2 = 1
time = 60000 p1 = 0 p2 = 0
time = 65000 p1 = 1 p2 = 0
time = 70000 p1 = 1 p2 = 0
time = 75000 p1 = 0 p2 = 1
time = 80000 p1 = 0 p2 = 0
time = 85000 p1 = 0 p2 = 0
time = 90000 p1 = 1 p2 = 0
time = 95000 p1 = 0 p2 = 1
time = 100000 p1 = 0 p2 = 0
two_decoder_test.v:26: $finish called at 100000 (ps)
time = 100000 p1 = 0 p2 = 0
```

 


Figure: Output from iverilog

Figure: Timing Diagram in GTKWave

Executing 1x4 Demux

■ Using iverilog

- Open the terminal
- Go to the directory containing verilog codes
- Type `iverilog -o demux_four demux_four.v demux_four_test.v`
- Type `vvp demux_four`

■ Using GTKWave

- In the terminal type `gtkwave demux_four_test.vcd &`
- Click on `demux_four_test` in the left pane of the pop up window
- Drag and drop all the signals into waveform window
- Go to *Time > Zoom > Zoom Best Fit* to see the whole waveform

```
Abhishek@Abhishek-Inspiron:~/Documents/demux$ iverilog -o demux_four demux_four.v demux_four_test.v
Abhishek@Abhishek-Inspiron:~/Documents/demux$ vvp demux_four
vpi_info: dumpfile demux_four_test.vcd opened for output:
time = 0 y = 0 a = 0 b = 0 c = 0 d = 0
time = 50000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 100000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 150000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 200000 y = 1 a = 0 b = 0 c = 0 d = 0
time = 250000 y = 1 a = 0 b = 1 c = 0 d = 0
time = 300000 y = 1 a = 0 b = 0 c = 1 d = 0
time = 350000 y = 1 a = 0 b = 0 c = 0 d = 1
time = 400000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 450000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 500000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 550000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 600000 y = 1 a = 1 b = 0 c = 0 d = 0
time = 650000 y = 1 a = 0 b = 1 c = 0 d = 0
time = 700000 y = 1 a = 0 b = 0 c = 1 d = 0
time = 750000 y = 1 a = 0 b = 0 c = 0 d = 1
time = 800000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 850000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 900000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 950000 y = 0 a = 0 b = 0 c = 0 d = 0
time = 1000000 y = 1 a = 1 b = 0 c = 0 d = 0
demux_four_test.v:33: $finish called at 1000000 (pps)
time = 1000000 y = 1 a = 1 b = 0 c = 0 d = 0
```

Figure: Output from iverilog

 


Figure: Timing Diagram in GTKWave

Executing D-Flip flop

- Using **iverilog**
 - Open the terminal
 - Go to the directory containing verilog codes
 - Type *iverilog -o dff dff.v dff_test.v*
 - Type *vvp dff*
- Using **GTKWave**
 - In the terminal type *gtkwave dff_test.vcd &*
 - Click on *dff_test* in the left pane of the pop up window
 - Drag and drop all the signals into waveform window
 - Go to *Time > Zoom > Zoom Best Fit* to see the whole waveform

```
Aravindkaran@inspiren-5370:~/Documents/dff_codes$ iverilog -o dff dff.v dff_test.v
Aravindkaran@inspiren-5370:~/Documents/dff_codes$ vvp dff
vcd info: dumpfile dff_test.vcd opened for output.
time = 0 rst = 0 D = 0 Q = 0
time = 10000 rst = 1 D = 1 Q = 0
time = 20000 rst = 1 D = 0 Q = 0
time = 30000 rst = 1 D = 1 Q = 1
time = 40000 rst = 0 D = 0 Q = 0
time = 50000 rst = 0 D = 1 Q = 0
time = 60000 rst = 1 D = 0 Q = 0
time = 70000 rst = 1 D = 1 Q = 1
time = 80000 rst = 0 D = 0 Q = 0
time = 90000 rst = 0 D = 1 Q = 0
dff_test.v[2]: $finish called at 100000 (1ps)
time = 100000 rst = 1 D = 0 Q = 0
```

Figure: Output from iverilog

 


Figure: Timing Diagram in GTKWave

References

- For any queries in **Verilog** refer to :
<http://www.asic-world.com/verilog/veritut.html>
- **Icarus Verilog** : <http://iverilog.icarus.com/>
- **GTKWave** : <http://gtkwave.sourceforge.net/>